

**DIPLOMA EXAMINATION IN ENGINEERING/TECHNOLOGY/  
MANAGEMENT/COMMERCIAL PRACTICE — APRIL, 2019**

**DIGITAL ELECTRONICS AND MICROPROCESSORS**

[Time : 3 hours

(Maximum marks : 100)

PART — A

(Maximum marks : 10)

Marks

I Answer *all* questions in one or two sentences. Each question carries 2 marks.

1. Draw the symbol of EX-OR gate and write output expression.
2. State Demorgan's theorems.
3. Name the different types of shift registers .
4. Name any two status flags used in 8085 Microprocessor.
5. State any two type of analog to digital converter.

(5×2 = 10)

PART — B

(Maximum marks : 30)

II Answer any *five* of the following questions. Each question carries 6 marks.

1. Convert the following Hexadecimal numbers into binary and then to decimal
  - (a) 4BC<sub>H</sub>
  - (b) F24<sub>H</sub>
2. Diagrammatically represent the following gates using NAND gate.
  - (a) AND
  - (b) OR
3. Draw the logic diagram and truth table of an active high clocked RS flip flop.
4. Draw the logic diagram and truth table of a serial-in parallel out shift register to store and retrieve a data 1011<sub>2</sub> using positive edge triggered D-flip flops.
5. List the characteristics of ECL logic family.
6. Draw a 2-bit synchronous up counter with truth table.
7. State any six highlighting features of 8085 Microprocessor.

(5×6 = 30)

## PART — C

(Maximum marks : 60)

(Answer *one* full question from each unit. Each full question carries 15 marks.)

## UNIT — I

- III (a) Convert +14 and +24 into binary equivalent and subtract +14 from + 24 using 2's complement method. Show all conversion steps. 8
- (b) Draw a two input AND gate using diodes and resistor and explain it. 7

OR

- IV (a) Convert the following decimal numbers to binary and hexadecimal number systems.  
(i)  $25.25_{10}$  (ii)  $61.625_{10}$  Show all conversion steps. 8
- (b) Explain the following characteristics of digital ICs.  
(i) Propagation delay (ii) Fan-in (iii) Fan out 7

## UNIT — II

- V Design and Draw the logic diagram for a full Adder using k-map. 15

OR

- VI (a) Draw the logic diagram and truth table to explain a 1 line to 4 line de-multiplexer. 9
- (b) Define a decoder. Draw and explain a basic binary decoder to detect  $1001_2$ . 6

## UNIT — III

- VII Explain a 4-bit (MOD-16) asynchronous up counter with the help of a logic diagram, timing diagram and a table showing counting sequence. 15

OR

- VIII Describe binary weighted type digital to analog converter with relevant diagrams. Prove the output voltage is proportional to the binary weights of resistors. 15

## UNIT — IV

- IX (a) Draw pin diagram of 8085 microprocessor and mark pin functions. 9
- (b) Explain the Flag register with reference to 8085 microprocessor. 6

OR

- X (a) Explain the following control and status signals in 8085 microprocessor.  
(i)  $S_0, S_1$  (ii)  $IO/\overline{M}$  (iii)  $\overline{RD}$  and  $\overline{WR}$  9
- (b) List the following instruction types in 8085 microprocessor with examples.  
(i) Data Transfer Instructions (ii) Arithmetic Instructions (iii) Logical Instructions. 6